

FIFTH EDITION

Fundamentals of Electric Circuits

**INSTRUCTOR
SOLUTIONS
MANUAL**



Charles K. Alexander | Matthew N. O. Sadiku

Chapter 1, Solution 1

(a) $q = 6.482 \times 10^{17} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-103.84 \text{ mC}}$

(b) $q = 1.24 \times 10^{18} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-198.65 \text{ mC}}$

(c) $q = 2.46 \times 10^{19} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-3.941 \text{ C}}$

(d) $q = 1.628 \times 10^{20} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-26.08 \text{ C}}$

Chapter 1, Solution 2

- (a) $i = dq/dt = 3 \text{ mA}$
- (b) $i = dq/dt = (16t + 4) \text{ A}$
- (c) $i = dq/dt = (-3e^{-t} + 10e^{-2t}) \text{ nA}$
- (d) $i = dq/dt = 1200\pi \cos 120\pi t \text{ pA}$
- (e) $i = dq/dt = -e^{-4t} (80 \cos 50t + 1000 \sin 50t) \mu\text{A}$

Chapter 1, Solution 3

$$(a) \quad q(t) = \int i(t)dt + q(0) = \underline{(3t + 1) \text{ C}}$$

$$(b) \quad q(t) = \int (2t + s) dt + q(v) = \underline{(t^2 + 5t) \text{ mC}}$$

$$(c) \quad q(t) = \int 20 \cos (10t + \pi / 6) + q(0) = \underline{(2 \sin(10t + \pi / 6) + 1) \mu\text{C}}$$

$$(d) \quad q(t) = \int 10e^{-30t} \sin 40t + q(0) = \frac{10e^{-30t}}{900 + 1600} (-30 \sin 40t - 40 \cos t)$$
$$= \underline{-e^{-30t} (0.16 \cos 40t + 0.12 \sin 40t) \text{ C}}$$

Chapter 1, Solution 4

$$q = it = 7.4 \times 20 = \underline{\underline{148 \text{ C}}}$$

Chapter 1, Solution 5

$$q = \int i dt = \int_0^{10} \frac{1}{2} t dt = \frac{t^2}{4} \Big|_0^{10} = \underline{\underline{25 \text{ C}}}$$

Chapter 1, Solution 6

(a) At $t = 1\text{ms}$, $i = \frac{dq}{dt} = \frac{30}{2} = \underline{\underline{15\text{ A}}}$


(b) At $t = 6\text{ms}$, $i = \frac{dq}{dt} = \underline{\underline{0\text{ A}}}$

(c) At $t = 10\text{ms}$, $i = \frac{dq}{dt} = \frac{-30}{4} = \underline{\underline{-7.5\text{ A}}}$

Chapter 1, Solution 7

$$i = \frac{dq}{dt} = \begin{cases} 25\text{A}, & 0 < t < 2 \\ -25\text{A}, & 2 < t < 6 \\ 25\text{A}, & 6 < t < 8 \end{cases}$$

which is sketched below:

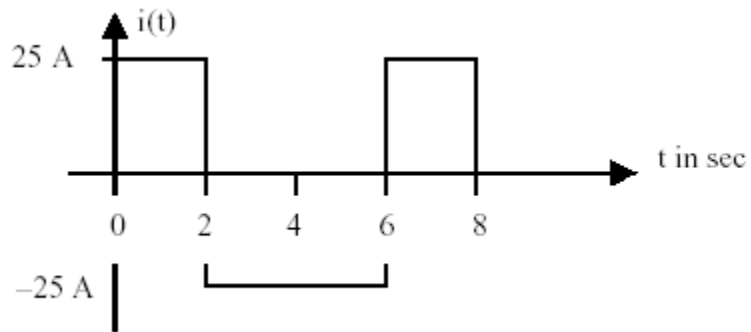

Chapter 1, Solution 8

$$q = \int i dt = \frac{10 \times 1}{2} + 10 \times 1 = \underline{15 \mu\text{C}}$$

Chapter 1, Solution 9

$$(a) \quad q = \int i dt = \int_0^1 10 dt = \underline{10 C}$$

$$(b) \quad q = \int_0^3 i dt = 10 \times 1 + \left(10 - \frac{5 \times 1}{2}\right) + 5 \times 1 \\ = 15 + 7.5 + 5 = \underline{22.5 C}$$

$$(c) \quad q = \int_0^5 i dt = 10 + 10 + 10 = \underline{30 C}$$

Chapter 1, Solution 10

$$q = it = 10 \times 10^3 \times 15 \times 10^{-6} = \underline{\underline{150 \text{ mC}}}$$

Chapter 1, Solution 11

$$q = it = 90 \times 10^{-3} \times 12 \times 60 \times 60 = \mathbf{3.888 \text{ kC}}$$

$$E = pt = ivt = qv = 3888 \times 1.5 = \mathbf{5.832 \text{ kJ}}$$

Chapter 1, Solution 12

For $0 < t < 6\text{s}$, assuming $q(0) = 0$,

$$q(t) = \int_0^t i dt + q(0) = \int_0^t 3t dt + 0 = 1.5t^2$$

$$\text{At } t=6, q(6) = 1.5(6)^2 = 54$$

For $6 < t < 10\text{s}$,

$$q(t) = \int_6^t i dt + q(6) = \int_6^t 18 dt + 54 = 18t - 54$$

$$\text{At } t=10, q(10) = 180 - 54 = 126$$

For $10 < t < 15\text{s}$,

$$q(t) = \int_{10}^t i dt + q(10) = \int_{10}^t (-12) dt + 126 = -12t + 246$$

$$\text{At } t=15, q(15) = -12 \times 15 + 246 = 66$$


For $15 < t < 20\text{s}$,

$$q(t) = \int_{15}^t 0 dt + q(15) = 66$$

Thus,

$$q(t) = \begin{cases} 1.5t^2 \text{ C, } 0 < t < 6\text{s} \\ 18t - 54 \text{ C, } 6 < t < 10\text{s} \\ -12t + 246 \text{ C, } 10 < t < 15\text{s} \\ 66 \text{ C, } 15 < t < 20\text{s} \end{cases}$$

The plot of the charge is shown below.

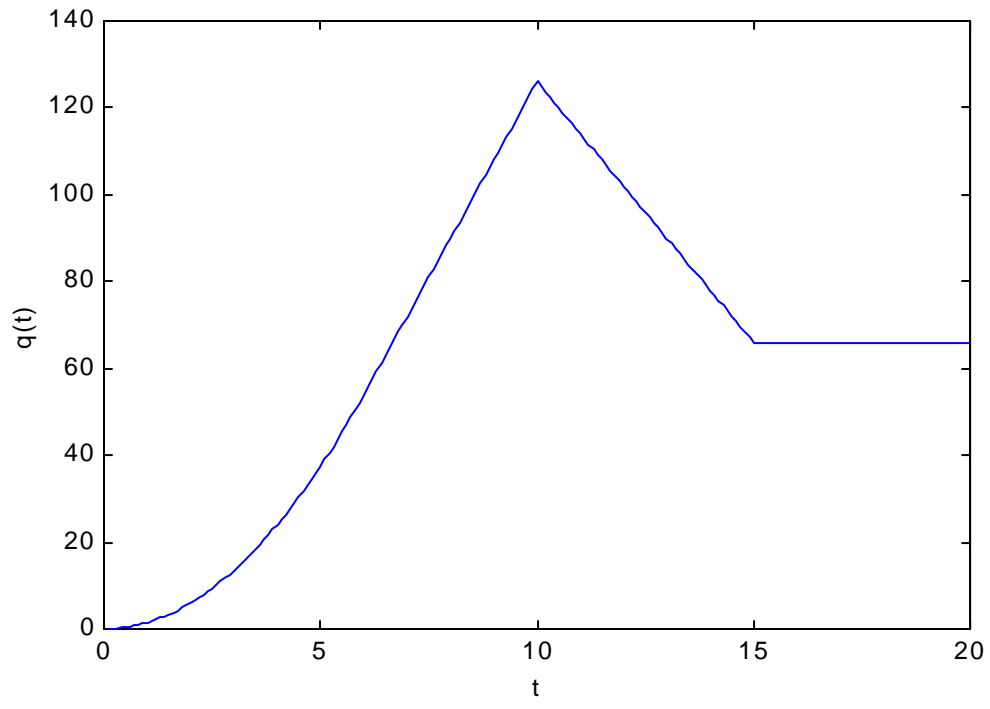

Chapter 1, Solution 13

$$(a) \quad i = [dq/dt] = 20\pi\cos(4\pi t) \text{ mA}$$

$$p = vi = 60\pi\cos^2(4\pi t) \text{ mW}$$

At $t=0.3\text{s}$,

$$p = vi = 60\pi\cos^2(4\pi \cdot 0.3) \text{ mW} = \mathbf{123.37 \text{ mW}}$$

$$(b) \quad W = \int p dt = 60\pi \int_0^{0.6} \cos^2(4\pi t) dt = 30\pi \int_0^{0.6} [1 + \cos(8\pi t)] dt$$

$$W = 30\pi[0.6 + (1/(8\pi))[\sin(8\pi \cdot 0.6) - \sin(0)]] = \mathbf{58.76 \text{ mJ}}$$

Chapter 1, Solution 14

$$(a) \quad q = \int i dt = \int_0^1 0.02(1 - e^{-0.5t}) dt = 0.02(t + 2e^{-0.5t}) \Big|_0^1 = 0.02(1 + 2e^{-0.5} - 2) = \mathbf{4.261 \text{ mC}}$$

$$(b) \quad p(t) = v(t)i(t) \\ p(1) = 10\cos(2) \times 0.02(1 - e^{-0.5}) = (-4.161)(0.007869) \\ = \mathbf{-32.74 \text{ mW}}$$

Chapter 1, Solution 15

$$\begin{aligned} \text{(a)} \quad q &= \int i dt = \int_0^2 0.006e^{-2t} dt = \left. \frac{-0.006}{2} e^{2t} \right|_0^2 \\ &= -0.003(e^{-4} - 1) = \\ &\quad \mathbf{2.945 \text{ mC}} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad v &= \frac{10di}{dt} = -0.012e^{-2t}(10) = -0.12e^{-2t} \text{ V this leads to } p(t) = v(t)i(t) = \\ &(-0.12e^{-2t})(0.006e^{-2t}) = \mathbf{-720e^{-4t} \mu\text{W}} \end{aligned}$$

$$\text{(c)} \quad w = \int pdt = -0.72 \int_0^3 e^{-4t} dt = \left. \frac{-720}{-4} e^{-4t} 10^{-6} \right|_0^3 = \mathbf{-180 \mu\text{J}}$$

Chapter 1, Solution 16


(a)

$$i(t) = \begin{cases} 30t \text{ mA}, & 0 < t < 2 \\ 120 - 30t \text{ mA}, & 2 < t < 4 \end{cases}$$

$$v(t) = \begin{cases} 5 \text{ V}, & 0 < t < 2 \\ -5 \text{ V}, & 2 < t < 4 \end{cases}$$

$$p(t) = \begin{cases} 150t \text{ mW}, & 0 < t < 2 \\ -600 + 150t \text{ mW}, & 2 < t < 4 \end{cases}$$

which is sketched below.

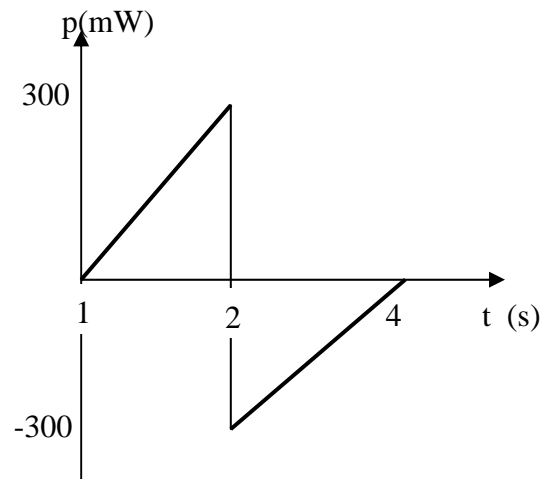

(b) From the graph of p ,

$$W = \int_0^4 p dt = \underline{0 \text{ J}}$$

Chapter 1, Solution 17

$$\sum p = 0 \rightarrow -205 + 60 + 45 + 30 + p_3 = 0$$

$$p_3 = 205 - 135 = 70 \text{ W}$$

Thus element 3 receives **70 W**.

Chapter 1, Solution 18

$$p_1 = 30(-10) = \mathbf{-300\ W}$$

$$p_2 = 10(10) = \mathbf{100\ W}$$

$$p_3 = 20(14) = \mathbf{280\ W}$$

$$p_4 = 8(-4) = \mathbf{-32\ W}$$

$$p_5 = 12(-4) = \mathbf{-48\ W}$$

Chapter 1, Solution 19

$$I = 8 - 2 = \mathbf{6\ A}$$

Calculating the power absorbed by each element means we need to find v_i for each element.

$$\begin{aligned} p_{8\ \text{amp source}} &= -8 \times 9 = \mathbf{-72\ W} \\ p_{\text{element with 9 volts across it}} &= 2 \times 9 = \mathbf{18\ W} \\ p_{\text{element with 3 volts across it}} &= 3 \times 6 = \mathbf{18\ W} \\ p_{6\ \text{volt source}} &= 6 \times 6 = \mathbf{36\ W} \end{aligned}$$

One check we can use is that the sum of the power absorbed must equal zero which is what it does.

Chapter 1, Solution 20

$$p_{30 \text{ volt source}} = 30 \times (-6) = \mathbf{-180 \text{ W}}$$

$$p_{12 \text{ volt element}} = 12 \times 6 = \mathbf{72 \text{ W}}$$

$$p_{28 \text{ volt element with 2 amps flowing through it}} = 28 \times 2 = \mathbf{56 \text{ W}}$$

$$p_{28 \text{ volt element with 1 amp flowing through it}} = 28 \times 1 = \mathbf{28 \text{ W}}$$

$$p_{\text{the } 5I_o \text{ dependent source}} = 5 \times 2 \times (-3) = \mathbf{-30 \text{ W}}$$

Since the total power absorbed by all the elements in the circuit must equal zero, or $0 = -180 + 72 + 56 + 28 - 30 + p_{\text{into the element with } V_o}$ or

$$p_{\text{into the element with } V_o} = 180 - 72 - 56 - 28 + 30 = \mathbf{54 \text{ W}}$$

Since $p_{\text{into the element with } V_o} = V_o \times 3 = 54 \text{ W}$ or $V_o = \mathbf{18 \text{ V}}$.

Chapter 1, Solution 21

$$p = vi \quad \longrightarrow \quad i = \frac{p}{v} = \frac{60}{120} = 0.5 \text{ A}$$

$$q = it = 0.5 \times 24 \times 60 \times 60 = \mathbf{43.2 \text{ kC}}$$

$$N_e = q \times 6.24 \times 10^{18} = \underline{2.696 \times 10^{23} \text{ electrons}}$$

Chapter 1, Solution 22

$$q = it = 40 \times 10^3 \times 1.7 \times 10^{-3} = \mathbf{68 \text{ C}}$$

Chapter 1, Solution 23

$$W = pt = 1.8 \times (15/60) \times 30 \text{ kWh} = 13.5 \text{ kWh}$$

$$C = 10 \text{ cents} \times 13.5 = \mathbf{\$1.35}$$

Chapter 1, Solution 24

$$W = pt = 60 \times 24 \text{ Wh} = 0.96 \text{ kWh} = 1.44 \text{ kWh}$$

$$C = 8.2 \text{ cents} \times 0.96 = \mathbf{11.808 \text{ cents}}$$

Chapter 1, Solution 25

$$\text{Cost} = 1.5 \text{ kW} \times \frac{3.5}{60} \text{ hr} \times 30 \times 8.2 \text{ cents/kWh} = \mathbf{21.52 \text{ cents}}$$

Chapter 1, Solution 26

(a) $i = \frac{0.8\text{A} \cdot \text{h}}{10\text{h}} = \mathbf{80\text{ mA}}$

(b) $p = vi = 6 \times 0.08 = \mathbf{0.48\text{ W}}$

(c) $w = pt = 0.48 \times 10\text{ Wh} = \mathbf{0.0048\text{ kWh}}$

Chapter 1, Solution 27

(a) Let $T = 4h = 4 \times 3600$

$$q = \int i dt = \int_0^T 3 dt = 3T = 3 \times 4 \times 3600 = \underline{43.2 \text{ kC}}$$

(b) $W = \int p dt = \int_0^T v i dt = \int_0^T (3) \left(10 + \frac{0.5t}{3600} \right) dt$

$$= 3 \left(10t + \frac{0.25t^2}{3600} \right) \Bigg|_0^{4 \times 3600} = 3[40 \times 3600 + 0.25 \times 16 \times 3600]$$
$$= \underline{475.2 \text{ kJ}}$$

(c) $W = 475.2 \text{ kWs}, \quad (J = \text{Ws})$

$$\text{Cost} = \frac{475.2}{3600} \text{ kWh} \times 9 \text{ cent} = \underline{1.188 \text{ cents}}$$

Chapter 1, Solution 28

$$(a) \quad i = \frac{P}{V} = \frac{60}{120}$$

$$= \mathbf{500 \text{ mA}}$$

$$(b) \quad W = pt = 60 \times 365 \times 24 \text{ Wh} = 525.6 \text{ kWh}$$

$$\text{Cost} = \$0.095 \times 525.6$$

$$= \mathbf{\$49.93}$$

Chapter 1, Solution 29

$$w = pt = 1.2\text{kW} \frac{(20 + 40 + 15 + 45)}{60} \text{hr} + 1.8\text{kW} \left(\frac{30}{60} \right) \text{hr}$$

$$= 2.4 + 0.9 = 3.3\text{kWh}$$

$$\text{Cost} = 12 \text{ cents} \times 3.3 = \underline{39.6 \text{ cents}}$$

Chapter 1, Solution 30

Monthly charge = \$6

First 250 kWh @ \$0.02/kWh = \$5

Remaining 2,436–250 kWh = 2,186 kWh @ \$0.07/kWh = \$153.02

Total = **\$164.02**

Chapter 1, Solution 31

$$\text{Total energy consumed} = 365(120 \times 4 + 60 \times 8) \text{ W}$$

$$\text{Cost} = \$0.12 \times 365 \times 960 / 1000 = \mathbf{\$42.05}$$

Chapter 1, Solution 32

$$i = 20 \mu\text{A}$$

$$q = 15 \text{ C}$$

$$t = q/i = 15/(20 \times 10^{-6}) = \mathbf{750 \times 10^3 \text{ hrs}}$$

Chapter 1, Solution 33

$$i = \frac{dq}{dt} \rightarrow q = \int i dt = 2000 \times 3 \times 10^{-3} = \underline{6 \text{ C}}$$

Chapter 1, Solution 34

(a) Energy = $\sum pt = 200 \times 6 + 800 \times 2 + 200 \times 10 + 1200 \times 4 + 200 \times 2$
 = **10 kWh**

(b) Average power = $10,000/24 = \mathbf{416.7 \text{ W}}$

Chapter 1, Solution 35

$$\text{energy} = (5 \times 5 + 4 \times 5 + 3 \times 5 + 8 \times 5 + 4 \times 10) / 60 = \mathbf{2.333 \text{ MWhr}}$$

Chapter 1, Solution 36

$$(a) \quad i = \frac{160\text{A} \cdot \text{h}}{40} = \underline{4 \text{ A}}$$

$$(b) \quad t = \frac{160\text{Ah}}{0.001\text{A}} = \frac{160,000\text{h}}{24\text{h / day}} = \underline{6,667 \text{ days}}$$

Chapter 1, Solution 37

$$W = pt = vit = 12 \times 40 \times 60 \times 60 = \mathbf{1.728 \text{ MJ}}$$

Chapter 1, Solution 38

$$P = 10 \text{ hp} = 7460 \text{ W}$$

$$W = pt = 7460 \times 30 \times 60 \text{ J} = \mathbf{13.43 \times 10^6 \text{ J}}$$

Chapter 1, Solution 39

$$W = pt = 600 \times 4 = 2.4 \text{ kWh}$$

$$C = 10 \text{ cents} \times 2.4 = \mathbf{24 \text{ cents}}$$

Chapter 2, Solution 1. Design a problem, complete with a solution, to help students to better understand Ohm's Law. Use at least two resistors and one voltage source. Hint, you could use both resistors at once or one at a time, it is up to you. Be creative.

Although there is no correct way to work this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

The voltage across a 5-k Ω resistor is 16 V. Find the current through the resistor.

Solution

$$v = iR \quad i = v/R = (16/5) \text{ mA} = \mathbf{3.2 \text{ mA}}$$

Chapter 2, Solution 2

$$p = v^2/R \rightarrow \mathbf{R} = v^2/p = 14400/60 = \mathbf{240 \text{ ohms}}$$

Chapter 2, Solution 3

For silicon, $\rho = 6.4 \times 10^2 \Omega\text{-m}$. $A = \pi r^2$. Hence,

$$R = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2} \longrightarrow r^2 = \frac{\rho L}{\pi R} = \frac{6.4 \times 10^2 \times 4 \times 10^{-2}}{\pi \times 240} = 0.033953$$

$$r = \mathbf{184.3 \text{ mm}}$$

Chapter 2, Solution 4

(a) $i = 40/100 = \mathbf{400 \text{ mA}}$

(b) $i = 40/250 = \mathbf{160 \text{ mA}}$

Chapter 2, Solution 5

$$\mathbf{n = 9; \quad l = 7; \quad \mathbf{b} = n + l - 1 = 15}$$

Chapter 2, Solution 6

$$n = 12; \quad l = 8; \quad \mathbf{b} = n + l - 1 = \underline{\mathbf{19}}$$

Chapter 2, Solution 7

6 branches and 4 nodes


Chapter 2, Solution 8. Design a problem, complete with a solution, to help other students to better understand Kirchhoff's Current Law. Design the problem by specifying values of i_a , i_b , and i_c , shown in Fig. 2.72, and asking them to solve for values of i_1 , i_2 , and i_3 . Be careful specify realistic currents.

Although there is no correct way to work this problem, this is an example based on the same kind of problem asked in the third edition.

Problem

Use KCL to obtain currents i_1 , i_2 , and i_3 in the circuit shown in Fig. 2.72.

Solution

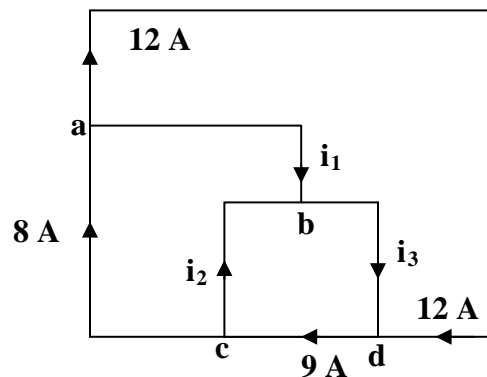

$$\begin{array}{lll} \text{At node a,} & 8 = 12 + i_1 \longrightarrow & \underline{i_1 = -4A} \\ \text{At node c,} & 9 = 8 + i_2 \longrightarrow & \underline{i_2 = 1A} \\ \text{At node d,} & 9 = 12 + i_3 \longrightarrow & \underline{i_3 = -3A} \end{array}$$

Chapter 2, Solution 9

$$\text{At A, } 1+6-i_1 = 0 \text{ or } i_1 = 1+6 = \mathbf{7 \text{ A}}$$

$$\text{At B, } -6+i_2+7 = 0 \text{ or } i_2 = 6-7 = \mathbf{-1 \text{ A}}$$

$$\text{At C, } 2+i_3-7 = 0 \text{ or } i_3 = 7-2 = \mathbf{5 \text{ A}}$$