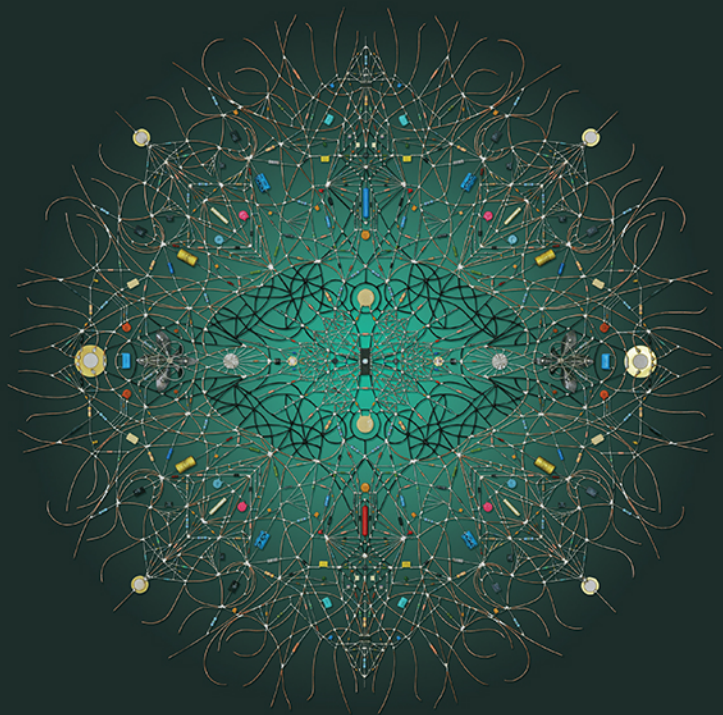


# ELECTRIC CIRCUITS



NILSSON • RIEDEL

12th Edition



# ELECTRIC CIRCUITS

TWELFTH EDITION

*This page intentionally left blank*

# ELECTRIC CIRCUITS

TWELFTH EDITION

James W. Nilsson

*Professor Emeritus  
Iowa State University*

Susan A. Riedel

*Associate Professor Emerita  
Marquette University*



**Content Development:** Erin Ault

**Content Production:** Rose Kernan, Scott Disanno,  
Pallavi Pandit, Siddharth Singh.

**Product Management:** Holly Stark

**Product Marketing:** Krista Clark

**Rights and Permissions:** Tanvi Bhatia / Anjali Sing

**Cover Image:** (C) Leonardo Ulian, Technological  
mandala 122—Radial itself

**Copyright © 2023, 2019, 2015 Pearson Education, Inc. or its affiliates, 221 River Street, Hoboken, NJ 07030.** All Rights Reserved. Manufactured in the United States of America. This publication is protected by copyright, and permission should be obtained from the publisher prior to any prohibited reproduction, storage in a retrieval system, or transmission in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise. For information regarding permissions, request forms, and the appropriate contacts within the Pearson Education Global Rights and Permissions department, please visit [www.pearsoned.com/permissions/](http://www.pearsoned.com/permissions/).

Microsoft and/or its respective suppliers make no representations about the suitability of the information contained in the documents and related graphics published as part of the services for any purpose. All such documents and related graphics are provided “as is” without warranty of any kind. Microsoft and/or its respective suppliers hereby disclaim all warranties and conditions with regard to this information, including all warranties and conditions of merchantability, whether express, implied or statutory, fitness for a particular purpose, title and non-infringement. In no event shall Microsoft and/or its respective suppliers be liable for any special, indirect or consequential damages or any damages whatsoever resulting from loss of use, data or profits, whether in an action of contract, negligence or other tortious action, arising out of or in connection with the use or performance of information available from the services.

The documents and related graphics contained herein could include technical inaccuracies or typographical errors. Changes are periodically added to the information herein. Microsoft and/or its respective suppliers may make improvements and/or changes in the product(s) and/or the program(s) described herein at any time. Partial screen shots may be viewed in full within the software version specified.

Microsoft® and Windows® are registered trademarks of the Microsoft Corporation in the U.S.A. and other countries. This book is not sponsored or endorsed by or affiliated with the Microsoft Corporation.

MATLAB is a registered trademark of The MathWorks, Inc. 3 Apple Hill Road, Natick, MA.

PSPICE is a registered trademark of Cadence Design Systems, 2655 Seely Avenue, San Jose, CA.

Multisim is a registered trademark of National Instruments, 11500 North MoPac Expwy, Austin, TX.

PEARSON, ALWAYS LEARNING, and MASTERING are exclusive trademarks owned by Pearson Education, Inc. or its affiliates in the U.S. and/or other countries.

Unless otherwise indicated herein, any third-party trademarks, logos, or icons that may appear in this work are the property of their respective owners, and any references to third-party trademarks, logos, icons, or other trade dress are for demonstrative or descriptive purposes only. Such references are not intended to imply any sponsorship, endorsement, authorization, or promotion of Pearson’s products by the owners of such marks, or any relationship between the owner and Pearson Education, Inc., or its affiliates, authors, licensees, or distributors.

#### **Library of Congress Cataloging-in-Publication Data**

Names: Nilsson, James William, author. | Riedel, Susan A., author.

Title: Electric circuits / James W. Nilsson, professor Emeritus Iowa State University, Susan A. Riedel, associate professor Emerita Marquette University.

Description: Twelfth edition. | Hoboken : Pearson, [2022] | Includes index.

| Summary: “Twelve edition of popular introductory electric circuits textbook including updated and new assessment problems and end-of-chapter problems” — Provided by publisher.

Identifiers: LCCN 2021058091 | ISBN 9780137648375 (hardcover)

Subjects: LCSH: Electric circuits.

Classification: LCC TK454 .N54 2022 | DDC 621.319/2—dc23/eng/20220113

LC record available at <https://lccn.loc.gov/2021058091>

ScoutAutomatedPrintCode

#### **Rental**

**ISBN-10:** 0-13-764837-5

**ISBN-13:** 978-0-13-764837-5

#### **Print Offer**

**ISBN-10:** 0-13-764843-X

**ISBN-13:** 978-0-13-764843-6



For Anna

*This page intentionally left blank*

# Brief Contents

	List of Examples	xii
	List of Tables	xvi
	List of Analysis Methods	xvii
	Preface	xx
<b>Chapter 1</b>	Circuit Variables	2
<b>Chapter 2</b>	Circuit Elements	26
<b>Chapter 3</b>	Simple Resistive Circuits	58
<b>Chapter 4</b>	Techniques of Circuit Analysis	92
<b>Chapter 5</b>	The Operational Amplifier	150
<b>Chapter 6</b>	Inductance, Capacitance, and Mutual Inductance	182
<b>Chapter 7</b>	Response of First-Order <i>RL</i> and <i>RC</i> Circuits	220
<b>Chapter 8</b>	Natural and Step Responses of <i>RLC</i> Circuits	272
<b>Chapter 9</b>	Sinusoidal Steady-State Analysis	318
<b>Chapter 10</b>	Sinusoidal Steady-State Power Calculations	374
<b>Chapter 11</b>	Balanced Three-Phase Circuits	412
<b>Chapter 12</b>	Introduction to the Laplace Transform	444
<b>Chapter 13</b>	The Laplace Transform in Circuit Analysis	482
<b>Chapter 14</b>	Introduction to Frequency-Selective Circuits	536
<b>Chapter 15</b>	Active Filter Circuits	572
<b>Chapter 16</b>	Fourier Series	618
<b>Chapter 17</b>	The Fourier Transform	662
<b>Chapter 18</b>	Two-Port Circuits	694
<b>Appendix A</b>	The Solution of Linear Simultaneous Equations	720
<b>Appendix B</b>	Complex Numbers	729
<b>Appendix C</b>	More on Magnetically Coupled Coils and Ideal Transformers	735
<b>Appendix D</b>	The Decibel	743
<b>Appendix E</b>	Bode Diagrams	745
<b>Appendix F</b>	An Abbreviated Table of Trigonometric Identities	759
<b>Appendix G</b>	An Abbreviated Table of Integrals	760
<b>Appendix H</b>	Common Standard Component Values	762
	Index	763



# Contents

List of Examples xii

List of Tables xvi

List of Analysis Methods xvii

Preface xx

## Chapter 1 Circuit Variables 2

*Practical Perspective: Balancing Power* 3

1.1 Electrical Engineering: An Overview 4

1.2 The International System of Units 9

1.3 Circuit Analysis: An Overview 11

1.4 Voltage and Current 12

1.5 The Ideal Basic Circuit Element 14

1.6 Power and Energy 15

*Practical Perspective: Balancing Power* 18

*Summary* 19

*Problems* 20

## Chapter 2 Circuit Elements 26

*Practical Perspective: Heating with Electric Radiators* 27

2.1 Voltage and Current Sources 28

2.2 Electrical Resistance (Ohm's Law) 32

2.3 Constructing a Circuit Model 36

2.4 Kirchhoff's Laws 39

2.5 Analyzing a Circuit Containing Dependent Sources 45

*Practical Perspective: Heating with Electric Radiators* 48

*Summary* 49

*Problems* 50

## Chapter 3 Simple Resistive Circuits 58

*Practical Perspective: Resistive Touch Screens* 59

3.1 Resistors in Series 60

3.2 Resistors in Parallel 61

3.3 The Voltage-Divider and Current-Divider Circuits 64

3.4 Voltage Division and Current Division 68

3.5 Measuring Voltage and Current 70

3.6 Measuring Resistance—The Wheatstone Bridge 73

3.7 Delta-to-Wye (Pi-to-Tee) Equivalent Circuits 75

*Practical Perspective: Resistive Touch*

*Screens* 78

*Summary* 79

*Problems* 80

## Chapter 4 Techniques of Circuit Analysis 92

*Practical Perspective: Circuits with Realistic Resistors* 93

4.1 Terminology 94

4.2 Introduction to the Node-Voltage Method 96

4.3 The Node-Voltage Method and Dependent Sources 98

4.4 The Node-Voltage Method: Some Special Cases 100

4.5 Introduction to the Mesh-Current Method 104

4.6 The Mesh-Current Method and Dependent Sources 107

4.7 The Mesh-Current Method: Some Special Cases 108

4.8 The Node-Voltage Method Versus the Mesh-Current Method 112

4.9 Source Transformations 115

4.10 Thévenin and Norton Equivalents 118

4.11 More on Deriving the Thévenin Equivalent 123

4.12 Maximum Power Transfer 126

4.13 Superposition 129

*Practical Perspective: Circuits with Realistic Resistors* 131

*Summary* 134

*Problems* 136

## Chapter 5 The Operational Amplifier 150

*Practical Perspective: Strain Gages* 151

5.1 Operational Amplifier Terminals 152

5.2 Terminal Voltages and Currents 152

5.3 The Inverting-Amplifier Circuit 156

5.4 The Summing-Amplifier Circuit 158

5.5 The Noninverting-Amplifier Circuit 160

5.6 The Difference-Amplifier Circuit 162

5.7 A More Realistic Model for the Operational Amplifier 167

<i>Practical Perspective: Strain Gages</i>	171
<i>Summary</i>	172
<i>Problems</i>	173

## Chapter 6 Inductance, Capacitance, and Mutual Inductance 182

*Practical Perspective: Capacitive Touch Screens* 183

6.1	The Inductor	184
6.2	The Capacitor	189
6.3	Series-Parallel Combinations of Inductance and Capacitance	194
6.4	Mutual Inductance	199
6.5	A Closer Look at Mutual Inductance	203
	<i>Practical Perspective: Capacitive Touch Screens</i>	209
	<i>Summary</i>	211
	<i>Problems</i>	212

## Chapter 7 Response of First-Order $RL$ and $RC$ Circuits 220

*Practical Perspective: Artificial Pacemaker* 221

7.1	The Natural Response of an $RL$ Circuit	222
7.2	The Natural Response of an $RC$ Circuit	228
7.3	The Step Response of $RL$ and $RC$ Circuits	233
7.4	A General Solution for Step and Natural Responses	241
7.5	Sequential Switching	246
7.6	Unbounded Response	250
7.7	The Integrating Amplifier	252
	<i>Practical Perspective: Artificial Pacemaker</i>	255
	<i>Summary</i>	256
	<i>Problems</i>	256

## Chapter 8 Natural and Step Responses of $RLC$ Circuits 272

*Practical Perspective: Clock for Computer Timing* 273

8.1	Introduction to the Natural Response of a Parallel $RLC$ Circuit	274
8.2	The Forms of the Natural Response of a Parallel $RLC$ Circuit	278
8.3	The Step Response of a Parallel $RLC$ Circuit	289
8.4	The Natural and Step Responses of a Series $RLC$ Circuit	296
8.5	A Circuit with Two Integrating Amplifiers	303
	<i>Practical Perspective: Clock for Computer Timing</i>	308
	<i>Summary</i>	309
	<i>Problems</i>	310

## Chapter 9 Sinusoidal Steady-State Analysis 318

*Practical Perspective: A Household Distribution Circuit* 319

9.1	The Sinusoidal Source	320
9.2	The Sinusoidal Response	323
9.3	The Phasor	324
9.4	The Passive Circuit Elements in the Frequency Domain	327
9.5	Kirchhoff's Laws in the Frequency Domain	332
9.6	Series, Parallel, and Delta-to-Wye Simplifications	333
9.7	Source Transformations and Thévenin–Norton Equivalent Circuits	340
9.8	The Node-Voltage Method	344
9.9	The Mesh-Current Method	345
9.10	The Transformer	347
9.11	The Ideal Transformer	351
9.12	Phasor Diagrams	357

*Practical Perspective: A Household Distribution Circuit* 359

*Summary* 361  
*Problems* 362

## Chapter 10 Sinusoidal Steady-State Power Calculations 374

*Practical Perspective: Vampire Power* 375

10.1	Instantaneous Power	376
10.2	Average and Reactive Power	377
10.3	The RMS Value and Power Calculations	382
10.4	Complex Power	384
10.5	Power Calculations	386
10.6	Maximum Power Transfer	393

*Practical Perspective: Vampire Power* 399

*Summary* 401  
*Problems* 401

## Chapter 11 Balanced Three-Phase Circuits 412

*Practical Perspective: Transmission and Distribution of Electric Power* 413

11.1	Balanced Three-Phase Voltages	414
11.2	Three-Phase Voltage Sources	415
11.3	Analysis of the Wye-Wye Circuit	416
11.4	Analysis of the Wye-Delta Circuit	422
11.5	Power Calculations in Balanced Three-Phase Circuits	425
11.6	Measuring Average Power in Three-Phase Circuits	430

*Practical Perspective: Transmission and Distribution of Electric Power* 433  
*Summary* 435  
*Problems* 436

*Practical Perspective: Pushbutton Telephone Circuits* 564  
*Summary* 564  
*Problems* 565

**Chapter 12 Introduction to the Laplace Transform 444**

*Practical Perspective: Transient Effects* 445  
**12.1** Definition of the Laplace Transform 446  
**12.2** The Step Function 447  
**12.3** The Impulse Function 449  
**12.4** Functional Transforms 452  
**12.5** Operational Transforms 453  
**12.6** Applying the Laplace Transform 458  
**12.7** Inverse Transforms 460  
**12.8** Poles and Zeros of  $F(s)$  470  
**12.9** Initial- and Final-Value Theorems 472  
*Practical Perspective: Transient Effects* 474  
*Summary* 476  
*Problems* 477

**Chapter 13 The Laplace Transform in Circuit Analysis 482**

*Practical Perspective: Surge Suppressors* 483  
**13.1** Circuit Elements in the  $s$  Domain 484  
**13.2** Circuit Analysis in the  $s$  Domain 486  
**13.3** Applications 488  
**13.4** The Transfer Function 500  
**13.5** The Transfer Function in Partial Fraction Expansions 502  
**13.6** The Transfer Function and the Convolution Integral 505  
**13.7** The Transfer Function and the Steady-State Sinusoidal Response 511  
**13.8** The Impulse Function in Circuit Analysis 514  
*Practical Perspective: Surge Suppressors* 520  
*Summary* 521  
*Problems* 522

**Chapter 14 Introduction to Frequency-Selective Circuits 536**

*Practical Perspective: Pushbutton Telephone Circuits* 537  
**14.1** Some Preliminaries 538  
**14.2** Low-Pass Filters 539  
**14.3** High-Pass Filters 545  
**14.4** Bandpass Filters 550  
**14.5** Bandreject Filters 560

**Chapter 15 Active Filter Circuits 572**

*Practical Perspective: Bass Volume Control* 573  
**15.1** First-Order Low-Pass and High-Pass Filters 574  
**15.2** Scaling 577  
**15.3** Op Amp Bandpass and Bandreject Filters 580  
**15.4** Higher-Order Op Amp Filters 587  
**15.5** Narrowband Bandpass and Bandreject Filters 600  
*Practical Perspective: Bass Volume Control* 605  
*Summary* 608  
*Problems* 609

**Chapter 16 Fourier Series 618**

*Practical Perspective: Active High-Q Filters* 619  
**16.1** Fourier Series Analysis: An Overview 621  
**16.2** The Fourier Coefficients 622  
**16.3** The Effect of Symmetry on the Fourier Coefficients 625  
**16.4** An Alternative Trigonometric Form of the Fourier Series 631  
**16.5** An Application 633  
**16.6** Average-Power Calculations with Periodic Functions 639  
**16.7** The rms Value of a Periodic Function 641  
**16.8** The Exponential Form of the Fourier Series 642  
**16.9** Amplitude and Phase Spectra 645  
*Practical Perspective: Active High-Q Filters* 647  
*Summary* 649  
*Problems* 650

**Chapter 17 The Fourier Transform 662**

*Practical Perspective: Filtering Digital Signals* 663  
**17.1** The Derivation of the Fourier Transform 664  
**17.2** The Convergence of the Fourier Integral 666  
**17.3** Using Laplace Transforms to Find Fourier Transforms 668  
**17.4** Fourier Transforms in the Limit 670

- 17.5** Some Mathematical Properties 673
- 17.6** Operational Transforms 674
- 17.7** Circuit Applications 679
- 17.8** Parseval's Theorem 681
  - Practical Perspective: Filtering Digital Signals* 687
  - Summary* 688
  - Problems* 688

## **Chapter 18** Two-Port Circuits 694

*Practical Perspective: Characterizing an Unknown Circuit* 695

- 18.1** The Terminal Equations 696
- 18.2** The Two-Port Parameters 697
- 18.3** Analysis of the Terminated Two-Port Circuit 705
- 18.4** Interconnected Two-Port Circuits 710
  - Practical Perspective: Characterizing an Unknown Circuit* 713
  - Summary* 714
  - Problems* 715

## **Appendix A** The Solution of Linear Simultaneous Equations 720

- A.1 Preliminary Steps 720
- A.2 Calculator and Computer Methods 721
- A.3 Paper-and-Pencil Methods 723
- A.4 Applications 725

## **Appendix B** Complex Numbers 729

- B.1 Notation 729
- B.2 The Graphical Representation of a Complex Number 730
- B.3 Arithmetic Operations 731
- B.4 Useful Identities 732
- B.5 The Integer Power of a Complex Number 733
- B.6 The Roots of a Complex Number 733

## **Appendix C** More on Magnetically Coupled Coils and Ideal Transformers 735

- C.1 Equivalent Circuits for Magnetically Coupled Coils 735
- C.2 The Need for Ideal Transformers in the Equivalent Circuits 739

## **Appendix D** The Decibel 743

## **Appendix E** Bode Diagrams 745

- E.1 Real, First-Order Poles and Zeros 745
- E.2 Straight-Line Amplitude Plots 746
- E.3 More Accurate Amplitude Plots 749
- E.4 Straight-Line Phase Angle Plots 750
- E.5 Bode Diagrams: Complex Poles and Zeros 752
- E.6 Straight-Line Amplitude Plots for Complex Poles 753
- E.7 Correcting Straight-Line Amplitude Plots for Complex Poles 754
- E.8 Phase Angle Plots for Complex Poles 756

## **Appendix F** An Abbreviated Table of Trigonometric Identities 759

## **Appendix G** An Abbreviated Table of Integrals 760

## **Appendix H** Common Standard Component Values 762

## **Index** 763

# List of Examples

## Chapter 1

- 1.1 Using SI Units and Prefixes for Powers of 10 11
- 1.2 Relating Current and Charge 15
- 1.3 Using the Passive Sign Convention 17
- 1.4 Relating Voltage, Current, Power, and Energy 17

## Chapter 2

- 2.1 Testing Interconnections of Ideal Sources 30
- 2.2 Testing Interconnections of Ideal Independent and Dependent Sources 31
- 2.3 Calculating Voltage, Current, and Power for a Simple Resistive Circuit 34
- 2.4 Constructing a Circuit Model of a Flashlight 36
- 2.5 Constructing a Circuit Model Based on Terminal Measurements 38
- 2.6 Using Kirchhoff's Current Law 41
- 2.7 Using Kirchhoff's Voltage Law 42
- 2.8 Applying Ohm's Law and Kirchhoff's Laws to Find an Unknown Current 42
- 2.9 Constructing a Circuit Model Based on Terminal Measurements 43
- 2.10 Analyzing a Circuit with a Dependent Source 45
- 2.11 Applying Ohm's Law and Kirchhoff's Laws to Find an Unknown Voltage 46
- 2.12 Applying Ohm's Law and Kirchhoff's Law in an Amplifier Circuit 47

## Chapter 3

- 3.1 Applying Series-Parallel Simplification 62
- 3.2 Solving a Circuit Using Series-Parallel Simplification 63
- 3.3 Designing a Simple Voltage Divider 65
- 3.4 Adding a Resistive Load to a Voltage Divider 65
- 3.5 The Effect of Resistor Tolerance on the Voltage-Divider Circuit 66
- 3.6 Designing a Current-Divider Circuit 67
- 3.7 Using Voltage Division and Current Division to Solve a Circuit 69
- 3.8 Using a d'Arsonval Ammeter 71
- 3.9 Using a d'Arsonval Voltmeter 72

- 3.10 Using a Wheatstone Bridge to Measure Resistance 75
- 3.11 Applying a Delta-to-Wye Transform 77

## Chapter 4

- 4.1 Identifying Node, Branch, Mesh, and Loop in a Circuit 94
- 4.2 Using Essential Nodes and Essential Branches to Write Simultaneous Equations 95
- 4.3 Using the Node-Voltage Method 97
- 4.4 Using the Node-Voltage Method with Dependent Sources 99
- 4.5 Node-Voltage Analysis of the Amplifier Circuit 102
- 4.6 Using the Mesh-Current Method 106
- 4.7 Using the Mesh-Current Method with Dependent Sources 107
- 4.8 A Special Case in the Mesh-Current Method 108
- 4.9 Mesh-Current Analysis of the Amplifier Circuit 111
- 4.10 Understanding the Node-Voltage Method Versus Mesh-Current Method 113
- 4.11 Comparing the Node-Voltage and Mesh-Current Methods 114
- 4.12 Using Source Transformations to Solve a Circuit 116
- 4.13 Using Special Source Transformation Techniques 117
- 4.14 Finding a Thévenin Equivalent 120
- 4.15 Finding a Norton Equivalent 121
- 4.16 Finding the Thévenin Equivalent of a Circuit with a Dependent Source 122
- 4.17 Finding the Thévenin Equivalent Resistance Directly from the Circuit 123
- 4.18 Finding the Thévenin Equivalent Resistance Using a Test Source 124
- 4.19 Finding the Thévenin Equivalent of a Circuit with Dependent Sources and Resistors 124
- 4.20 Using a Thévenin Equivalent to Analyze the Amplifier Circuit 125
- 4.21 Calculating the Condition for Maximum Power Transfer 127
- 4.22 Using Superposition to Solve a Circuit 129
- 4.23 Using Superposition to Solve a Circuit with Dependent Sources 130



## Chapter 5

- 5.1 Analyzing an Op Amp Circuit 155
- 5.2 Designing an Inverting Amplifier 157
- 5.3 Designing a Summing Amplifier 159
- 5.4 Designing a Noninverting Amplifier 161
- 5.5 Designing a Difference Amplifier 163
- 5.6 Calculating the CMRR 167
- 5.7 Analyzing a Noninverting-Amplifier Circuit Using a Realistic Op Amp Model 169

## Chapter 6

- 6.1 Determining the Voltage, Given the Current, at the Terminals of an Inductor 184
- 6.2 Determining the Current, Given the Voltage, at the Terminals of an Inductor 186
- 6.3 Determining the Current, Voltage, Power, and Energy for an Inductor 187
- 6.4 Determining Current, Voltage, Power, and Energy for a Capacitor 191
- 6.5 Finding Finding  $v$ ,  $p$ , and  $w$  Induced by a Triangular Current Pulse for a Capacitor 192
- 6.6 Finding the Equivalent Inductance 196
- 6.7 Finding the Equivalent Capacitance 197
- 6.8 Finding Mesh-Current Equations for a Circuit with Magnetically Coupled Coils 201
- 6.9 Calculating the Coupling Coefficient and Stored Energy for Magnetically Coupled Coils 209

## Chapter 7

- 7.1 Determining the Natural Response of an  $RL$  Circuit 224
- 7.2 Determining the Natural Response of an  $RL$  Circuit with Parallel Inductors 227
- 7.3 Determining the Natural Response of an  $RC$  Circuit 230
- 7.4 Determining the Natural Response of an  $RC$  Circuit with Series Capacitors 231
- 7.5 Determining the Step Response of an  $RL$  Circuit 234
- 7.6 Determining the Step Response of an  $RC$  Circuit 239
- 7.7 Using the General Solution Method to Find an  $RL$  Circuit's Natural Response 242
- 7.8 Using the General Solution Method to Find an  $RC$  Circuit's Step Response 243
- 7.9 Using the General Solution Method to Find an  $RL$  Circuit's Step Response 244
- 7.10 Determining the Step Response of a Circuit with Magnetically Coupled Coils 245
- 7.11 Analyzing an  $RL$  Circuit That Has Sequential Switching 247

- 7.12 Analyzing an  $RC$  Circuit That Has Sequential Switching 249
- 7.13 Finding the Unbounded Response in an  $RC$  Circuit 251
- 7.14 Analyzing an Integrating Amplifier 253
- 7.15 Analyzing an Integrating Amplifier That Has Sequential Switching 253

## Chapter 8

- 8.1 Finding the Roots of the Characteristic Equation of a Parallel  $RLC$  Circuit 277
- 8.2 Finding the Overdamped Natural Response of a Parallel  $RLC$  Circuit 280
- 8.3 Calculating Branch Currents in the Natural Response of a Parallel  $RLC$  Circuit 281
- 8.4 Finding the Underdamped Natural Response of a Parallel  $RLC$  Circuit 284
- 8.5 Finding the Critically Damped Natural Response of a Parallel  $RLC$  Circuit 288
- 8.6 Finding the Overdamped Step Response of a Parallel  $RLC$  Circuit 293
- 8.7 Finding the Underdamped Step Response of a Parallel  $RLC$  Circuit 294
- 8.8 Finding the Critically Damped Step Response of a Parallel  $RLC$  Circuit 294
- 8.9 Comparing the Three-Step Response Forms 295
- 8.10 Finding Step Response of a Parallel  $RLC$  Circuit with Initial Stored Energy 295
- 8.11 Finding the Natural Response of a Series  $RLC$  Circuit 302
- 8.12 Finding the Step Response of a Series  $RLC$  Circuit 302
- 8.13 Analyzing Two Cascaded Integrating Amplifiers 305
- 8.14 Analyzing Two Cascaded Integrating Amplifiers with Feedback Resistors 307

## Chapter 9

- 9.1 Finding the Characteristics of a Sinusoidal Current 321
- 9.2 Finding the Characteristics of a Sinusoidal Voltage 322
- 9.3 Translating a Sine Expression to a Cosine Expression 322
- 9.4 Calculating the rms Value of a Triangular Waveform 322
- 9.5 Adding Cosines Using Phasors 326
- 9.6 Calculating Component Voltages Using Phasor Techniques 331
- 9.7 Using KVL in the Frequency Domain 333

- 9.8 Combining Impedances in Series 334
- 9.9 Combining Impedances in Series and in Parallel 337
- 9.10 Using a Delta-to-Wye Transform in the Frequency Domain 339
- 9.11 Performing Source Transformations in the Frequency Domain 341
- 9.12 Finding a Thévenin Equivalent in the Frequency Domain 342
- 9.13 Using the Node-Voltage Method in the Frequency Domain 344
- 9.14 Using the Mesh-Current Method in the Frequency Domain 346
- 9.15 Analyzing a Linear Transformer in the Frequency Domain 349
- 9.16 Analyzing an Ideal Transformer Circuit in the Frequency Domain 355
- 9.17 Using Phasor Diagrams to Analyze a Circuit 357
- 9.18 Using Phasor Diagrams to Analyze Capacitive Loading Effects 358

## Chapter 10

- 10.1 Calculating Average and Reactive Power 380
- 10.2 Making Power Calculations Involving Household Appliances 382
- 10.3 Determining Average Power Delivered to a Resistor by a Sinusoidal Voltage 384
- 10.4 Calculating Complex Power 385
- 10.5 Calculating Power Using Phasor Voltage and Current 387
- 10.6 Calculating Average and Reactive Power 389
- 10.7 Calculating Power in Parallel Loads 390
- 10.8 Balancing Power Delivered with Power Absorbed in an AC Circuit 391
- 10.9 Determining Maximum Power Transfer without Load Restrictions 395
- 10.10 Determining Maximum Power Transfer with Load Impedance Restriction 396
- 10.11 Finding Maximum Power Transfer with Impedance Angle Restrictions 396
- 10.12 Finding Maximum Power Transfer in a Circuit with an Ideal Transformer 397

## Chapter 11

- 11.1 Analyzing a Wye-Wye Circuit 420
- 11.2 Analyzing a Wye-Delta Circuit 423
- 11.3 Calculating Power in a Three-Phase Wye-Wye Circuit 428
- 11.4 Calculating Power in a Three-Phase Wye-Delta Circuit 428

- 11.5 Calculating Three-Phase Power with an Unspecified Load 429
- 11.6 Computing Wattmeter Readings in Three-Phase Circuits 432

## Chapter 12

- 12.1 Using Step Functions to Represent a Function of Finite Duration 448
- 12.2 Using Laplace Transforms to Predict a Circuit's Response 460
- 12.3 Finding the Inverse Laplace Transform When  $F(s)$  Has Distinct Real Roots 462
- 12.4 Finding the Inverse Laplace Transform When  $F(s)$  Has Distinct Complex Roots 465
- 12.5 Finding the Inverse Laplace Transform When  $F(s)$  Has Repeated Real Roots 467
- 12.6 Finding the Inverse Laplace Transform When  $F(s)$  Has Repeated Complex Roots 468
- 12.7 Finding the Inverse Laplace Transform of an Improper Rational Function 470
- 12.8 Finding and Plotting the Poles and Zeros of an  $s$ -Domain Function 471
- 12.9 Applying the Initial- and Final-Value Theorems 474

## Chapter 13

- 13.1 Transforming a Circuit into the  $s$  Domain 488
- 13.2 The Natural Response of an  $RC$  Circuit 489
- 13.3 The Step Response of an  $RLC$  Circuit 489
- 13.4 Analyzing a Circuit with a Sinusoidal Source 491
- 13.5 Analyzing a Circuit with Multiple Meshes 493
- 13.6 Creating a Thévenin Equivalent in the  $s$  Domain 495
- 13.7 Analyzing a Circuit with Mutual Inductance 497
- 13.8 Applying Superposition in the  $s$  Domain 499
- 13.9 Deriving the Transfer Function of a Circuit 501
- 13.10 Analyzing the Transfer Function of a Circuit 503
- 13.11 Using the Convolution Integral to Find an Output Signal 509
- 13.12 Using the Transfer Function to Find the Steady-State Sinusoidal Response 513
- 13.13 A Series Inductor Circuit with an Impulsive Response 515
- 13.14 A Circuit with Both Internally Generated and Externally Applied Impulses 518

## Chapter 14

- 14.1 Designing a Low-Pass Filter 543
- 14.2 Designing a Series  $RC$  Low-Pass Filter 544
- 14.3 Designing a Series  $RL$  High-Pass Filter 547

- 14.4** Loading the Series *RL* High-Pass Filter 548
- 14.5** Designing a Bandpass Filter 555
- 14.6** Designing a Parallel *RLC* Bandpass Filter 555
- 14.7** Determining the Effect of a Nonideal Voltage Source on a Series *RLC* Bandpass Filter 557
- 14.8** Designing a Series *RLC* Bandreject Filter 562

## Chapter 15

- 15.1** Designing a Low-Pass Op Amp Filter 575
- 15.2** Designing a High-Pass Op Amp Filter 576
- 15.3** Scaling a Series *RLC* Filter 578
- 15.4** Scaling a Prototype Low-Pass Op Amp Filter 579
- 15.5** Designing a Broadband Bandpass Op Amp Filter 583
- 15.6** Designing a Broadband Bandreject Op Amp Filter 586
- 15.7** Designing a Fourth-Order Low-Pass Active Filter 589
- 15.8** Calculating Butterworth Transfer Functions 592
- 15.9** Designing a Fourth-Order Low-Pass Butterworth Filter 594
- 15.10** Determining the Order of a Butterworth Filter 597
- 15.11** An Alternate Approach to Determining the Order of a Butterworth Filter 597
- 15.12** Designing a Butterworth Bandpass Filter 599
- 15.13** Designing a High-Q Bandpass Filter 602
- 15.14** Designing a High-Q Bandreject Filter 604

## Chapter 16

- 16.1** Finding the Fourier Series of a Triangular Waveform 623
- 16.2** Finding the Fourier Series of a Periodic Function with Symmetry 630
- 16.3** Calculating Forms of the Trigonometric Fourier Series for Periodic Voltage 632
- 16.4** Finding the Response of an *RLC* Circuit to a Square-Wave Voltage 637

- 16.5** Calculating Average Power for a Circuit with a Periodic Voltage Source 640
- 16.6** Estimating the rms Value of a Periodic Function 642
- 16.7** Finding the Exponential Form of the Fourier Series 644
- 16.8** Plotting the Amplitude and Phase Spectra for a Periodic Voltage 646

## Chapter 17

- 17.1** Finding the Fourier Transform of a Constant 667
- 17.2** Finding the Fourier Transform from the Laplace Transform 669
- 17.3** Deriving an Operational Fourier Transform 677
- 17.4** Using the Fourier Transform to Find the Transient Response 679
- 17.5** Using the Fourier Transform to Find the Sinusoidal Steady-State Response 680
- 17.6** Applying Parseval's Theorem 683
- 17.7** Applying Parseval's Theorem to an Ideal Bandpass Filter 684
- 17.8** Applying Parseval's Theorem to a Low-Pass Filter 685
- 17.9** Calculating Energy Contained in a Rectangular Voltage Pulse 686

## Chapter 18

- 18.1** Finding the *z* Parameters of a Two-Port Circuit 698
- 18.2** Finding the *a* Parameters from Measurements 699
- 18.3** Finding *h* Parameters from Measurements and Table 18.1 702
- 18.4** Determining Whether a Circuit Is Reciprocal and Symmetric 703
- 18.5** Analyzing a Terminated Two-Port Circuit 709
- 18.6** Analyzing Cascaded Two-Port Circuits 709



# List of Tables


- 1.1 The International System of Units (SI) 10
- 1.2 Derived Units in SI 10
- 1.3 Standardized Prefixes to Signify Powers of 10 10
- 1.4 Interpretation of Reference Directions in Fig. 1.5 14
- 1.5 Voltage and Current Values for the Circuit in Fig. 1.7 19
- 4.1 Terms for Describing Circuits 95
- 4.2 PSpice Sensitivity Analysis Results 133
- 4.3 Steps in the Node-Voltage Method and the Mesh-Current Method 135
- 6.1 Inductor and Capacitor Duality 198
- 7.1 Value of  $e^{-t/\tau}$  for  $t$  Equal to Integral Multiples of  $\tau$  226
- 8.1 Natural-Response Parameters of the Parallel  $RLC$  Circuit 276
- 8.2 Equations for Analyzing the Natural Response of Parallel  $RLC$  Circuits 288
- 8.3 Equations for Analyzing the Step Response of Parallel  $RLC$  Circuits 293
- 8.4 Equations for Analyzing the Natural Response of Series  $RLC$  Circuits 299
- 8.5 Equations for Analyzing the Step Response of Series  $RLC$  Circuits 301
- 9.1 Impedance and Reactance Values 331
- 9.2 Admittance and Susceptance Values 336
- 9.3 Impedance and Related Values 361
- 10.1 Annual Energy Requirements of Electric Household Appliances 381
- 10.2 Three Power Quantities and Their Units 385
- 10.3 Average Power Consumption of Common Electrical Devices 399
- 12.1 An Abbreviated List of Laplace Transform Pairs 453
- 12.2 An Abbreviated List of Operational Transforms 458
- 12.3 Four Useful Transform Pairs 469
- 13.1 Summary of the  $s$ -Domain Equivalent Circuits 486
- 14.1 Input and Output Voltage Magnitudes for Three Frequencies 543
- 15.1 Normalized (so that  $\omega_c = 1$  rad/s) Butterworth Polynomials up to the Eighth Order 593
- 17.1 Fourier Transforms of Elementary Functions 672
- 17.2 Operational Transforms 677
- 18.1 Parameter Conversion Table 701
- 18.2 Two-Port Parameter Relationships for Reciprocal Circuits 703
- 18.3 Terminated Two-Port Equations 706

# List of Analysis Methods

- Analysis Method 4.1:** The Basic Version of the Node-Voltage Method 97
- Analysis Method 4.2:** Modified Step 3 for the Node-Voltage Method 99
- Analysis Method 4.3:** Complete Form of the Node-Voltage Method 102
- Analysis Method 4.4:** The Basic Version of the Mesh-Current Method 105
- Analysis Method 4.5:** Modified Step 3 for the Mesh-Current Method 107
- Analysis Method 4.6:** Complete Form of the Mesh-Current Method 110
- Analysis Method 5.1:** Analyzing an Ideal Op Amp Circuit with a Negative Feedback Path 154
- Analysis Method 7.1:** Finding the  $RL$  Natural Response 224
- Analysis Method 7.2:** Finding the  $RC$  Natural Response 230
- Analysis Method 7.3:** Finding the  $RL$  Step Response 234
- Analysis Method 7.4:** Finding the  $RC$  Step Response 238
- Analysis Method 7.5:** Finding the  $RL$  and  $RC$  Natural and Step Response 242
- Analysis Method 8.1:** The Natural Response of an Overdamped Parallel  $RLC$  Circuit 280
- Analysis Method 8.2:** The Natural Response of an Overdamped or Underdamped Parallel  $RLC$  Circuit 283
- Analysis Method 8.3:** The Natural Response of Parallel  $RLC$  Circuits 287
- Analysis Method 8.4:** The Step Response of Parallel  $RLC$  Circuits 292
- Analysis Method 8.5:** The Natural Response of Series  $RLC$  Circuits 299
- Analysis Method 8.6:** The Step Response of Series  $RLC$  Circuits 301
- Analysis Method 13.1:** Laplace-Transform Circuit Analysis Method 487

# Combine this...

PART A

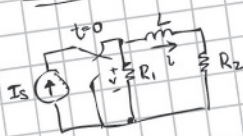

Given:  
 $I_s = 51.0 \text{ mA}$   
 $R_1 = 54.0 \text{ k}\Omega$   
 $R_2 = 51.0 \text{ k}\Omega$   
 $L = 51.0 \text{ mH}$

Find:  
 initial current  $i(0^-)$   
 before break switch



$$I_s = i$$

$$i = 51.0 \text{ mA}$$

Assume when circuit is in steady state, inductor acts as a short



Use Kirchoff's current law

$$I_s = i + i_R$$

$$I_s = i + \frac{V}{R}$$

$$I_s = i + \frac{iR_1}{R_2}$$

$$I_s = i \left( 1 + \frac{R_1}{R_2} \right)$$

$$I_s = i \left( 1 + \frac{R_1}{R_2} \right)$$

$$i = \frac{51.0 \text{ mA}}{\left( 1 + \frac{54.0 \text{ k}\Omega}{51.0 \text{ k}\Omega} \right)} = 24.77 \text{ mA}$$



# With the Power of Mastering Engineering for Electric Circuits 12/e

Mastering™ is the teaching and learning platform that empowers every student. By combining trusted authors' content with digital tools developed to engage students and emulate the office hours experience, Mastering personalizes learning and improves results for each student.

The screenshot displays the Mastering Engineering interface for a problem titled "The Natural Response of an RL Circuit".

**Learning Goal:**  
To analyze an RL circuit to determine the initial current through an inductor, the time constant, and the expression for the natural response of the inductor current, and to use the expression for the inductor current to find other circuit quantities, such as current, voltage, power, or energy.  
The natural response of an RL circuit is the response of the inductor current to the sudden removal of a DC source. When this occurs, the inductor releases the stored energy.

**Figure 1** (of 2): A circuit diagram showing a DC current source  $I_s$  in series with a switch. The switch is shown in the closed position at  $t = 0$ . The circuit includes a resistor  $R_1$  in parallel with the switch, and an inductor  $L$  in series with a resistor  $R_2$ . The current through the inductor is labeled  $i$ .

**Part A**  
For the given circuit (Figure 1), assume the make-before-break switch has been up for a long time and moves down at  $t = 0$ . Find the initial current through the inductor. Assume that  $I_s = 51.0 \text{ mA}$ ,  $R_1 = 51.0 \text{ k}\Omega$ ,  $R_2 = 51.0 \text{ k}\Omega$ , and  $L = 51.0 \text{ mH}$ .  
Express your answer to three significant figures and include the appropriate units.

**Input:**  $i(0^-) = i(0^+) = 51 \text{ mA}$

**Feedback:** Incorrect; Try Again; 4 attempts remaining. Note that elements in series have the same current but the inductor is not in series with the current source. Use Kirchhoff's current law or the current divider to find the initial inductor current.

## Empower Each Learner

Each student learns at a different pace. Personalized learning, including adaptive tools and wrong-answer feedback, pinpoints the precise areas where each student needs practice, giving all students the support they need — when and where they need it — to be successful.

Learn more at [www.pearson.com/mastering/engineering](http://www.pearson.com/mastering/engineering)

# Preface

The Twelfth Edition of *Electric Circuits* represents a planned, incremental revision focusing on the Assessment Problems and the end-of-chapter Problems. The fundamental goals of the text are unchanged. These goals are:

- To build new concepts and ideas on concepts previously presented. This challenges students to see the explicit connections among the many circuit analysis tools and methods.
- To develop problem-solving skills that rely on a solid conceptual foundation. This challenges students to examine many different approaches to solving a problem before writing a single equation.
- To introduce realistic engineering experiences at every opportunity. This challenges students to develop the insights of a practicing engineer and exposes them to practice of engineering.

## Why This Edition?

The Twelfth Edition of *Electric Circuits* incorporates the following new and revised elements:

- End-of-chapter problems—Problem solving is fundamental to the study of circuit analysis. Having a wide variety of problems to assign and work is a key to success in any circuits course. Therefore, nearly all of the existing existing end-of-chapter problems were revised, and some new end-of-chapter problems were added. The only problems that were not altered are those asking you to derive or prove a particular result.
- Assessment Problems—After most subsections in a chapter, one or two assessment problems give you a chance to reflect on the new material and apply it to solve a problem. Every assessment problem is new to the Twelfth Edition and comes with answers to all parts of the problem posed. Many of the assessment problems have interactive video solutions available in Mastering, which guide you through the solution and ask you to participate in the problem-solving process.
- Mastering Engineering is an online tutorial and assessment program that provides students with personalized feedback and hints and instructors with diagnostics to track students' progress. With the Twelfth Edition, Mastering Engineering will offer new enhanced end-of-chapter problems with hints and feedback, Coaching Activities, and Adaptive Follow-Up assignments. Visit [www.masteringengineering.com](http://www.masteringengineering.com) for more information.
- We have eliminated the Selected Answers appendix that has appeared in previous editions. Some instructors may not wish to assign problems whose solutions are readily available to students at the back of the text. Since instructors have the complete solutions available to them, they are free to supply answers to select problems they assign if they wish. Providing the reader with answers to problems discourages them from checking their own answers using an alternate analysis technique or comparing their answers to known circuit behavior.

## Hallmark Features

### Analysis Methods

Students encountering circuit analysis for the first time can benefit from step-by-step directions that lead them to a problem's solution. These directions are compiled into a collection of analysis methods, and many of the examples in the text use these analysis methods. Some of the analysis methods that are used most often can be found inside the book's covers for easy reference.

### Chapter Problems

Users of *Electric Circuits* have consistently praised the breadth, depth, variety, and sheer number of Chapter Problems. In the Twelfth Edition, there are nearly 1200 end-of-chapter problems, organized at the end of each chapter by section.

### Practical Perspectives

The Twelfth Edition continues using Practical Perspectives to introduce the chapter. They provide real-world circuit examples, taken from real-world devices. Every chapter begins by describing a practical application of the material that follows. After presenting that material, the chapter revisits the Practical Perspective, performing a quantitative circuit analysis using the newly introduced chapter material. End-of-chapter problems directly related to the Practical Perspective application are identified for easy reference. These problems provide additional opportunities for solving real-world problems using the chapter material.

### Assessment Problems

Each chapter begins with a set of chapter objectives. At key points in the chapter, you are asked to stop and assess your mastery of a particular objective by solving one or more assessment problems. The answers to the assessment problems are given at the conclusion of each problem, so you can check your work. If you can solve the assessment problems for a given objective, you have mastered that objective. The Student Study area of Mastering includes interactive video solutions for many of the assessment problems. If you want more practice, several end-of-chapter problems that relate to the objective are suggested at the conclusion of the assessment problems.

### Examples

Every chapter includes numeric examples illustrating the concepts presented in the text. There are nearly 200 examples in this text that apply a particular concept, often employ an Analysis Method, and exemplify good problem-solving skills.

### Checking the Results of Analysis

You are encouraged to check analysis results to verify that they make sense. There are many different ways to check results and examples of these checks are included throughout the text, the assessment problems, and the end-of-chapter problems. Don't rely on comparing your results with some known answer, and instead check your own answer by solving the problem in a different way or comparing your answer with known circuit behavior.

### Fundamental Equations and Concepts

Throughout the text, you will see fundamental equations and concepts set apart from the main text. This is done to help you focus on some of the key principles in electric circuits and to help you navigate through the important topics.



## Integration of Computer Tools

Computer tools can assist in the learning process by providing a visual representation of a circuit's behavior, validating a calculated solution, reducing the computational burden of more complex circuits, and iterating toward a desired solution using parameter variation. This computational support is often invaluable in the design process. The Twelfth Edition supports PSpice and Multisim, both popular computer tools for circuit simulation and analysis. Chapter problems suited for exploration with PSpice and Multisim are marked accordingly.

## Design Emphasis

The Twelfth Edition emphasizes the design of circuits in many ways. First, many of the Practical Perspective discussions focus on the design aspects of the circuits. The accompanying Chapter Problems continue discussing design issues in these practical examples. Second, design-oriented Chapter Problems have been labeled explicitly, enabling students and instructors to identify those problems with a design focus. Third, identifying problems suited to PSpice or Multisim exploration suggests design opportunities using these software tools. Fourth, some problems in nearly every chapter ask you to choose realistic circuit component values in achieving a desired circuit design. Once such a problem has been analyzed, the student can build and test the circuit in a laboratory, comparing the analysis with the measured performance of the actual circuit.

## Accuracy

All text and problems in the Twelfth Edition have undergone our strict hallmark accuracy checking process, to ensure the most error-free book possible.

## Resources for Students

**Mastering Engineering**—Mastering Engineering provides tutorial homework problems designed to emulate the instructor's office hour environment, guiding students through engineering concepts with self-paced individualized coaching. These in-depth tutorial homework problems provide students with feedback specific to their errors and optional hints that break problems down into simpler steps. Visit [www.pearson.com/mastering/engineering](http://www.pearson.com/mastering/engineering) for more information.

**Learning Catalytics**—Learning Catalytics is an interactive student response tool that encourages team-based learning by using students' smartphones, tablets, or laptops to engage them in interactive tasks and thinking. Visit [www.learningcatalytics.com](http://www.learningcatalytics.com) for more information.

**Student Workbook**—This resource teaches students techniques for solving problems presented in the text. Organized by concepts, this is a valuable problem-solving resource for students. The Student Workbook is available in Mastering.

**Introduction to Multisim and Introduction to PSpice Manuals**—There are several powerful circuit simulators available free or at low cost to students. Circuit simulation is an excellent tool for exploring a circuit in depth and for visualizing the behavior of a circuit. The Multisim and PSpice manuals introduce these two popular simulators using examples tied directly to the main text. These manuals are available in Mastering.

## Resources for Instructors

All instructor resources are available for download at [www.pearsonhighered.com](http://www.pearsonhighered.com). If you are in need of a login and password for this site, please contact your local Pearson representative.

**Instructor Solutions Manual**—Fully worked-out solutions to Assessment Problems and end-of-chapter problems.

**PowerPoint Lecture Images**—All figures from the text are available in PowerPoint for your lecture needs. An additional set of full lecture slides with embedded assessment questions are available upon request.

**Mastering Engineering**—This online tutorial and assessment program allows you to integrate dynamic homework with automated grading and personalized feedback. MasteringEngineering allows you to easily track the performance of your entire class on an assignment-by-assignment basis, or the detailed work of an individual student. For more information visit [www.masteringengineering.com](http://www.masteringengineering.com).

**Learning Catalytics**—This “bring your own device” student engagement, assessment, and classroom intelligence system enables you to measure student learning during class, and adjust your lectures accordingly. A wide variety of question and answer types allows you to author your own questions, or you can use questions from a library available in the system. For more information visit [www.learningcatalytics.com](http://www.learningcatalytics.com) or click on the Learning Catalytics link inside Mastering Engineering.

**Introduction to Multisim and Introduction to PSpice Manuals**—These manuals, available in Mastering, are excellent resources for those wishing to integrate PSpice or Multisim into their classes.

## Prerequisites

In writing the first 12 chapters of the text, we have assumed that the reader has taken a course in elementary differential and integral calculus. We have also assumed that the reader has had an introductory physics course, at either the high school or university level, that introduces the concepts of energy, power, electric charge, electric current, electric potential, and electromagnetic fields. In writing the final six chapters, we have assumed the student has had, or is enrolled in, an introductory course in differential equations.

## Course Options

The text has been designed for use in a one-semester, two-semester, or a three-quarter sequence.

- *Single-semester course:* After covering Chapters 1–4 and Chapters 6–10 (omitting Sections 7.7 and 8.5) the instructor can develop the desired emphasis by covering Chapter 5 (operational amplifiers), Chapter 11 (three-phase circuits), Chapters 13 and 14 (Laplace methods), or Chapter 18 (two-port circuits).
- *Two-semester sequence:* Assuming three lectures per week, cover the first nine chapters during the first semester, leaving Chapters 10–18 for the second semester.
- *Academic quarter schedule:* Cover Chapters 1–6 in the first quarter, Chapters 7–12 in the second quarter, and Chapters 13–18 in the third quarter.



Note that the introduction to operational amplifier circuits in Chapter 5 can be omitted with minimal effect on the remaining material. If Chapter 5 is omitted, you should also omit Section 7.7, Section 8.5, Chapter 15, and those assessment problems and end-of-chapter problems that pertain to operational amplifiers.

There are several appendixes at the end of the book to help readers make effective use of their mathematical background. Appendix A presents several different methods for solving simultaneous linear equations; complex numbers are reviewed in Appendix B; Appendix C contains additional material on magnetically coupled coils and ideal transformers; Appendix D contains a brief discussion of the decibel; Appendix E is dedicated to Bode diagrams; Appendix F is devoted to an abbreviated table of trigonometric identities that are useful in circuit analysis; and an abbreviated table of useful integrals is given in Appendix G. Appendix H provides tables of common standard component values for resistors, inductors, and capacitors, to be used in solving many end-of-chapter problems.

## Acknowledgments


Jim Nilsson has my eternal gratitude for inviting me to collaborate with him on this textbook. I learned so much from him about teaching and writing and hard work. It is a gift to be associated with him through this textbook, and to impact the education of the thousands of students who use this text.

The Eleventh Edition was a year-long undertaking to examine every word, sentence, paragraph, and chapter of this text to streamline, clarify, and modernize the writing and the presentation. Much to my horror, I forgot to thank the incredible Matt Walker, who served as the developmental editor on that project and made countless suggestions for improving both the content and the design. He was a great collaborator and I'm so very sorry for failing to catch this error before the Eleventh Edition was published.

There were many hard-working people behind the scenes at our publisher who deserve my thanks and gratitude for their efforts on behalf of the Twelfth Edition. A special shout-out to the amazing Rose Kernan, who has helped guide these revisions since the Seventh Edition, which first appeared in 2005. Rose is so easy to work with, does her very best to keep me on top of the production schedule, and is an endless source of encouragement. I would also like to thank Erin Ault, Erin Sullivan, Holly Stark, Sandra Rodriguez, and Scott Disanno at Pearson for their continued support, encouragement, and hard work. I thank the staff at Integra Software Solutions for their dedication and attention to detail in typesetting this text.

I am very grateful for the many instructors and students who have done formal reviews of the text or offered positive feedback and suggestions for improvement more informally. I am pleased to receive email from instructors and students who use the book, even when they are pointing out an error that I failed to catch in the review process. Thank you for taking the time to contact Pearson or me with your comments and suggestions. I use as many of them as possible to continue to improve the content, the pedagogy, and the presentation in this text. I am privileged to have the opportunity to impact the educational experience of the many thousands of future engineers who will use this text.

*SUSAN A. RIEDEL*

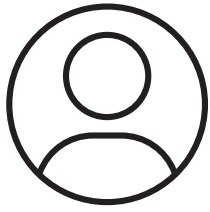

# Pearson's Commitment to Diversity, Equity, and Inclusion

**Pearson is dedicated to creating bias-free content that reflects the diversity, depth, and breadth of all learners' lived experiences.**

We embrace the many dimensions of diversity, including but not limited to race, ethnicity, gender, sex, sexual orientation, socioeconomic status, ability, age, and religious or political beliefs.

Education is a powerful force for equity and change in our world. It has the potential to deliver opportunities that improve lives and enable economic mobility. As we work with authors to create content for every product and service, we acknowledge our responsibility to demonstrate inclusivity and incorporate diverse scholarship so that everyone can achieve their potential through learning. As the world's leading learning company, we have a duty to help drive change and live up to our purpose to help more people create a better life for themselves and to create a better world.

## **Our ambition is to purposefully contribute to a world where:**

- Everyone has an equitable and lifelong opportunity to succeed through learning.
- Our educational content accurately reflects the histories and lived experiences of the learners we serve.
- Our educational products and services are inclusive and represent the rich diversity of learners.
- Our educational content prompts deeper discussions with students and motivates them to expand their own learning (and worldview).

## **Accessibility**

We are also committed to providing products that are fully accessible to all learners. As per Pearson's guidelines for accessible educational Web media, we test and retest the capabilities of our products against the highest standards for every release, following the WCAG guidelines in developing new products for copyright year 2022 and beyond.



You can learn more about Pearson's commitment to accessibility at

<https://www.pearson.com/us/accessibility.html>

## **Contact Us**

While we work hard to present unbiased, fully accessible content, we want to hear from you about any concerns or needs with this Pearson product so that we can investigate and address them.



Please contact us with concerns about any potential bias at

<https://www.pearson.com/report-bias.html>



For accessibility-related issues, such as using assistive technology with Pearson products, alternative text requests, or accessibility

documentation, email the Pearson Disability Support team at [disability.support@pearson.com](mailto:disability.support@pearson.com)



**Pearson**

*This page intentionally left blank*

# ELECTRIC CIRCUITS

TWELFTH EDITION

# CHAPTER

# 1

## CHAPTER CONTENTS

- 1.1 **Electrical Engineering: An Overview** *p. 4*
- 1.2 **The International System of Units** *p. 9*
- 1.3 **Circuit Analysis: An Overview** *p. 11*
- 1.4 **Voltage and Current** *p. 12*
- 1.5 **The Ideal Basic Circuit Element** *p. 14*
- 1.6 **Power and Energy** *p. 15*

## CHAPTER OBJECTIVES

- 1 Understand and be able to use SI units and the standard prefixes for powers of 10.
- 2 Know and be able to use the definitions of *voltage* and *current*.
- 3 Know and be able to use the definitions of *power* and *energy*.
- 4 Be able to use the passive sign convention to calculate the power for an ideal basic circuit element given its voltage and current.

## Circuit Variables

**Electrical engineering** is an exciting and challenging profession for anyone who has a genuine interest in, and aptitude for, applied science and mathematics. Electrical engineers play a dominant role in developing systems that change the way people live and work. Satellite communication links, cell phones, computers, televisions, diagnostic and surgical medical equipment, robots, and aircraft represent systems that define a modern technological society. As an electrical engineer, you can participate in this ongoing technological revolution by improving and refining existing systems and by discovering and developing new systems to meet the needs of our ever-changing society.

This text introduces you to electrical engineering using the analysis and design of linear circuits. We begin this chapter by presenting an overview of electrical engineering, some ideas about an engineering point of view as it relates to circuit analysis, and a review of the International System of Units. We then describe generally what circuit analysis entails. Next, we introduce the concepts of voltage and current. We continue by discussing the ideal basic element and the need for a polarity reference system. We conclude the chapter by describing how current and voltage relate to power and energy.

## ■ Practical Perspective

### Balancing Power

One of the most important skills you will develop is the ability to check your answers for the circuits you design and analyze using the tools developed in this text. A common method used to check for valid answers is to calculate the power in the circuit. The linear circuits we study have no net power, so the sum of the power associated with all circuit components must be zero. If the total power for the circuit is zero, we say that the power balances, but if the total power is not zero, we need to find the errors in our calculation.


As an example, we will consider a simple model for distributing electricity to a typical home. (Note that a

more realistic model will be investigated in the Practical Perspective for Chapter 9.) The components labeled a and b represent the source of electrical power for the home. The components labeled c, d, and e represent the wires that carry the electrical current from the source to the devices in the home requiring electrical power. The components labeled f, g, and h represent lamps, televisions, hair dryers, refrigerators, and other devices that require power.

Once we have introduced the concepts of voltage, current, power, and energy, we will examine this circuit model in detail, and use a power balance to determine whether the results of analyzing this circuit are correct.



romakoma/Shutterstock

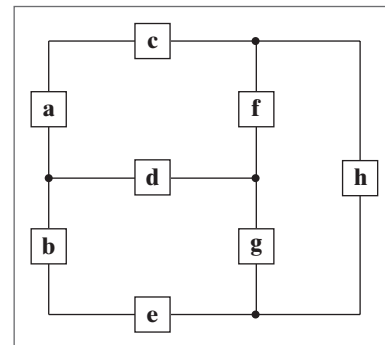

MasterPhoto/Shutterstock



Olga Yastremska/123RF

## 1.1 Electrical Engineering: An Overview


The electrical engineering profession focuses on systems that produce, transmit, and measure electric signals. Electrical engineering combines the physicist's models of natural phenomena with the mathematician's tools for manipulating those models to produce systems that meet practical needs. Electrical systems pervade our lives; they are found in homes, schools, workplaces, and transportation vehicles everywhere. We begin by presenting a few examples from each of the five major classifications of electrical systems:

- communication systems
- computer systems
- control systems
- power systems
- signal-processing systems

Then we describe how electrical engineers analyze and design such systems.

**Communication systems** are electrical systems that generate, transmit, and distribute information. Well-known examples include television equipment, such as cameras, transmitters, receivers, and monitors; radio telescopes, used to explore the universe; satellite systems, which return images of other planets and our own; radar systems, used to coordinate plane flights; and telephone systems.

Figure 1.1 depicts the major components of a modern telephone system that supports mobile phones, landlines, and international calling. Inside a telephone, a microphone turns sound waves into electric signals. These signals are carried to local or mobile exchanges, where they are

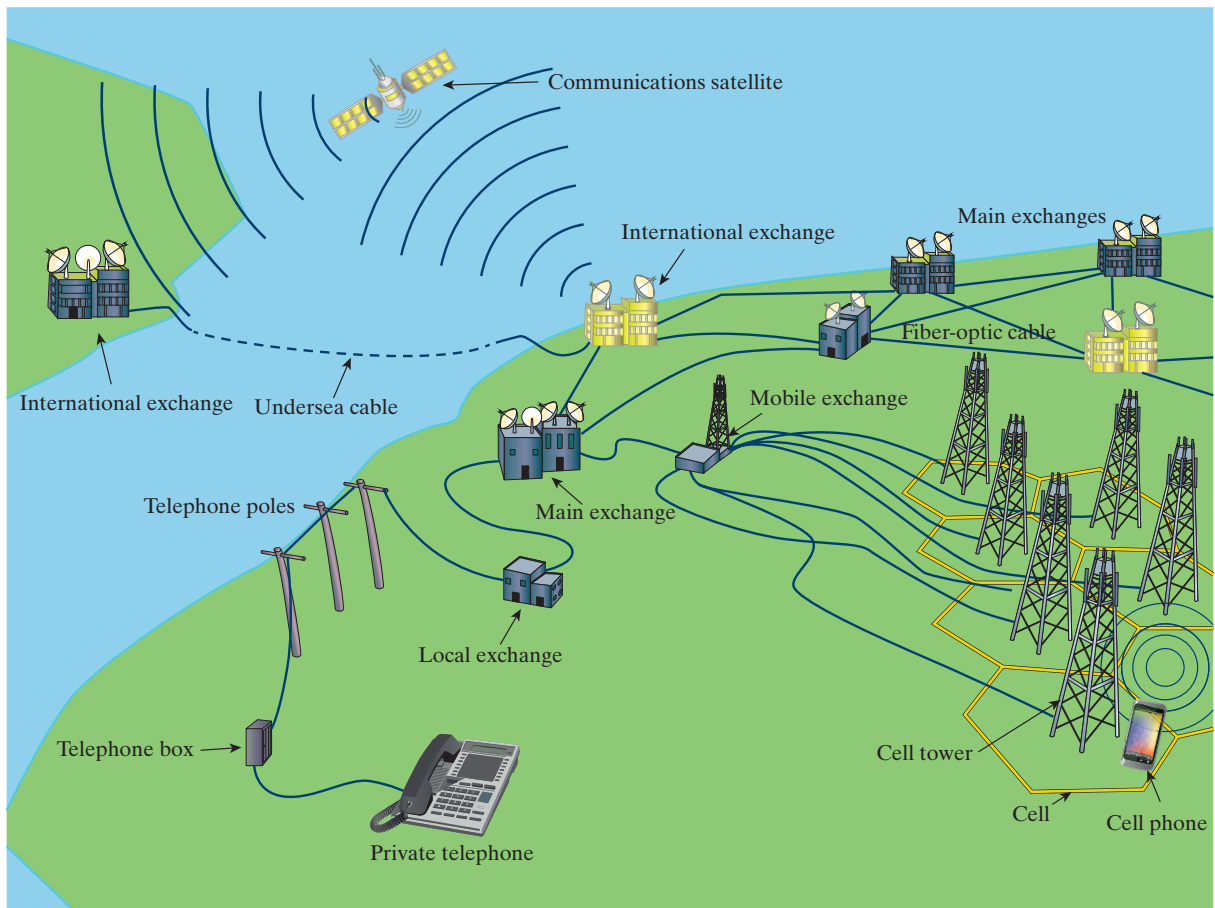

**Figure 1.1** ▲ A telephone system.



combined with the signals from tens, hundreds, or thousands of other telephones. The form of the signals can be radio waves traveling through air, electrical signals traveling in underground coaxial cable, light pulses traveling in fiber-optic cable, or microwave signals that travel through space. The combined signals are broadcast from a transmission antenna to a receiving antenna. There the combined signals are separated at an exchange, and each is routed to the appropriate telephone, where an earphone acts as a speaker to convert the received electric signals back into sound waves. At each stage of the process, electric circuits operate on the signals. Imagine the challenge involved in designing, building, and operating each circuit in a way that guarantees that all of the hundreds of thousands of simultaneous calls have high-quality connections.


**Computer systems** use electric signals to process information ranging from word processing to mathematical computations. Systems range in size and power from simple calculators to personal computers to supercomputers that perform such complex tasks as processing weather data and modeling chemical interactions of complex organic molecules. These systems include networks of integrated circuits—miniature assemblies of hundreds, thousands, or millions of electrical components that often operate at speeds and power levels close to fundamental physical limits, including the speed of light and the thermodynamic laws.

**Control systems** use electric signals to regulate processes. Examples include the control of temperatures, pressures, and flow rates in an oil refinery; the fuel–air mixture in a fuel-injected automobile engine; mechanisms such as the motors, doors, and lights in elevators; and the locks in the Panama Canal. The autopilot and autoland systems that help to fly and land airplanes are also familiar control systems.

**Power systems** generate and distribute electric power. Electric power, which is the foundation of our technology-based society, usually is generated in large quantities by nuclear, hydroelectric, solar, and thermal (coal-, oil-, or gas-fired) generators. Power is distributed by a grid of conductors that crisscross the country. A major challenge in designing and operating such a system is to provide sufficient redundancy and control so that failure of any piece of equipment does not leave a city, state, or region completely without power.

**Signal-processing systems** act on electric signals that represent information. They transform the signals and the information contained in them into a more suitable form. There are many different ways to process the signals and their information. For example, image-processing systems gather massive quantities of data from orbiting weather satellites, reduce the amount of data to a manageable level, and transform the remaining data into a video image for the evening news broadcast. A magnetic resonance imaging (MRI) scan is another example of an image-processing system. It takes signals generated by powerful magnetic fields and radio waves and transforms them into a detailed, three-dimensional image such as the one shown in Fig. 1.2, which can be used to diagnose disease and injury.

Considerable interaction takes place among the engineering disciplines involved in designing and operating these five classes of systems. Thus, communications engineers use digital computers to control the flow of information. Computers contain control systems, and control systems contain computers. Power systems require extensive communications systems to

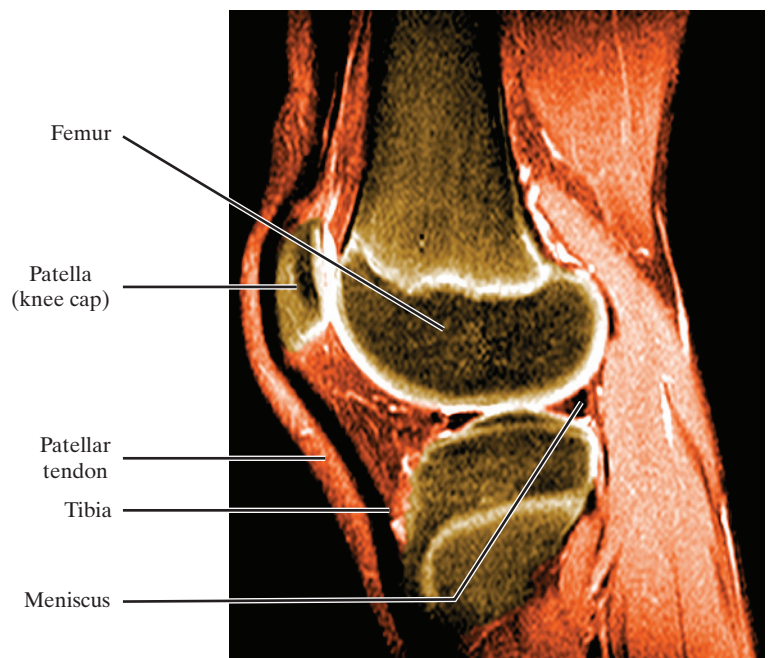


**Figure 1.2** ▲ An MRI scan of an adult knee joint.  
Science History Images/Alamy Stock Photo



coordinate safely and reliably the operation of components, which may be spread across a continent. A signal-processing system may involve a communications link, a computer, and a control system.

A good example of the interaction among systems is a commercial airplane, such as the one shown in Fig. 1.3. A sophisticated communications system enables the pilot and the air traffic controller to monitor the plane's location, permitting the air traffic controller to design a safe flight path for all of the nearby aircraft and enabling the pilot to keep the plane on its designated path. An onboard computer system manages engine functions, implements the navigation and flight control systems, and generates video information screens in the cockpit. A complex control system uses cockpit commands to adjust the position and speed of the airplane, producing the appropriate signals to the engines and the control surfaces (such as the wing flaps, ailerons, and rudder) to ensure the plane remains safely airborne and on the desired flight path. The plane must have its own power system to stay aloft and to provide and distribute the electric power needed to keep the cabin lights on, make the coffee, and activate the entertainment system. Signal-processing systems reduce the noise in air traffic communications and transform information about the plane's location into the more meaningful form of a video display in the cockpit. Engineering challenges abound in the design of each of these systems and their integration into a coherent whole. For example, these systems must operate in widely varying and unpredictable environmental conditions. Perhaps the most important engineering challenge is to guarantee that sufficient redundancy is incorporated in the designs, ensuring that passengers arrive safely and on time at their desired destinations.

Although electrical engineers may be interested primarily in one area, they must also be knowledgeable in other areas that interact with this area of interest. This interaction is part of what makes electrical engineering a challenging and exciting profession. The emphasis in engineering is on making things work, so an engineer is free to acquire and use any technique from any field that helps to get the job done.

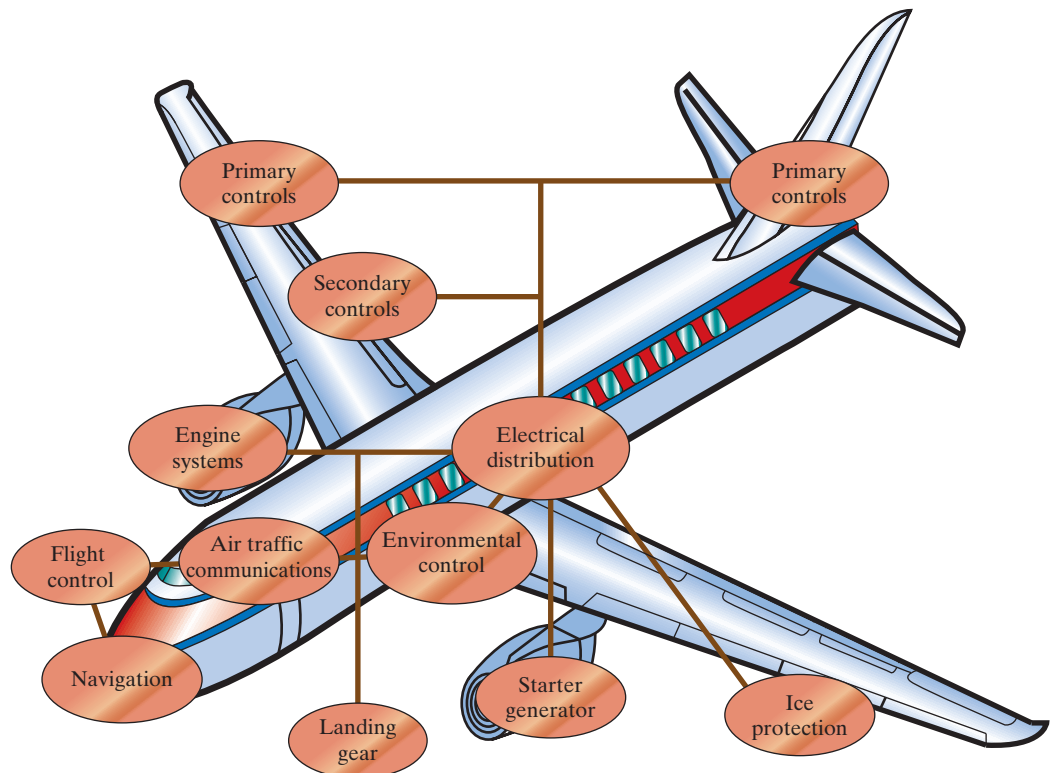

**Figure 1.3** ▲ Interacting systems on a commercial aircraft.

## Circuit Theory

An **electric circuit** is a mathematical model that approximates the behavior of an actual electrical system. Since electric circuits are found in every branch of electrical engineering, they provide an important foundation for learning how to design and operate systems such as those just described. The models, the mathematical techniques, and the language of circuit theory will form the intellectual framework for your future engineering endeavors.

Note that the term *electric circuit* is commonly used to refer to an actual electrical system as well as to the model that represents it. In this text, when we talk about an electric circuit, we always mean a model, unless otherwise stated. It is the modeling aspect of circuit theory that has broad applications across engineering disciplines.

**Circuit theory** is a special case of electromagnetic field theory: the study of static and moving electric charges. But applying generalized field theory to the study of electric signals is cumbersome and requires advanced mathematics. Consequently, a course in electromagnetic field theory is not a prerequisite to understanding the material in this text. We do, however, assume that you have had an introductory physics course in which electrical and magnetic phenomena were discussed.

Three basic assumptions permit us to use circuit theory, rather than electromagnetic field theory, to study a physical system represented by an electric circuit.

1. *Electrical effects happen instantaneously throughout a system.* We can make this assumption because we know that electric signals travel at or near the speed of light. Thus, if the system is physically small, electric signals move through it so quickly that we can consider them to affect every point in the system simultaneously. A system that is small enough so that we can make this assumption is called a **lumped-parameter system**.
2. *The net charge on every component in the system is always zero.* Thus, no component can collect a net excess of charge, although some components, as you will learn later, can hold equal but opposite separated charges.
3. *There is no magnetic coupling between the components in a system.* As we demonstrate later, magnetic coupling can occur *within* a component.

That's it; there are no other assumptions. Using circuit theory provides simple solutions (of sufficient accuracy) to problems that would become hopelessly complicated if we were to use electromagnetic field theory. These benefits are so great that engineers sometimes specifically design electrical systems to ensure that these assumptions are met. The importance of assumptions 2 and 3 becomes apparent after we introduce the basic circuit elements and the rules for analyzing interconnected elements.

Let's take a closer look at assumption 1. The question is, "How small does a physical system have to be to qualify as a lumped-parameter system?" To get a quantitative answer to this question, remember that electric signals propagate as waves. If the wavelength of the signal is large compared to the physical dimensions of the system, we have a lumped-parameter system. The wavelength  $\lambda$  is the velocity divided by the repetition rate, or **frequency**, of the signal; that is,  $\lambda = c/f$ . The frequency  $f$  is measured in hertz (Hz). For example, power systems in the United States operate at 60 Hz. If we use the speed of light ( $c = 3 \times 10^8$  m/s) as the velocity of propagation, the wavelength is  $5 \times 10^6$  m. If the power system of interest is physically smaller than this wavelength, we can represent it as a lumped-parameter system and use circuit theory to analyze its behavior.

How do we define *smaller*? A good rule is the *rule of 1/10th*: If the dimension of the system is less than 1/10th the dimension of the wavelength, you have a lumped-parameter system. Thus, as long as the physical dimension of the power system is less than  $5 \times 10^5$  m (which is about 310 miles), we can treat it as a lumped-parameter system.

Now consider a communication system that sends and receives radio signals. The propagation frequency of radio signals is on the order of  $10^9$  Hz, so the wavelength is 0.3 m. Using the rule of 1/10th, a communication system qualifies as a lumped-parameter system if its dimension is less than 3 cm. Whenever any of the pertinent physical dimensions of a system under study approaches the wavelength of its signals, we must use electromagnetic field theory to analyze that system. Throughout this text we study circuits derived from lumped-parameter systems.

## Problem Solving

As a practicing engineer, you will not be asked to solve problems that have already been solved. Whether you are improving the performance of an existing system or designing a new system, you will be working on unsolved problems. As a student, however, you will read and discuss problems with known solutions. Then, by solving related homework and exam problems on your own, you will begin to develop the skills needed to attack the unsolved problems you'll face as a practicing engineer.

Let's review several general problem-solving strategies. Many of these pertain to thinking about and organizing your solution strategy *before* proceeding with calculations.

1. *Identify what's given and what's to be found.* In problem solving, you need to know your destination before you can select a route for getting there. What is the problem asking you to solve or find? Sometimes the goal of the problem is obvious; other times you may need to paraphrase or make lists or tables of known and unknown information to see your objective.

On one hand, the problem statement may contain extraneous information that you need to weed out before proceeding. On the other hand, it may offer incomplete information or more complexities than can be handled by the solution methods you know. In that case, you'll need to make assumptions to fill in the missing information or simplify the problem context. Be prepared to circle back and reconsider supposedly extraneous information and/or your assumptions if your calculations get bogged down or produce an answer that doesn't seem to make sense.

2. *Sketch a circuit diagram or other visual model.* Translating a verbal problem description into a visual model is often a useful step in the solution process. If a circuit diagram is already provided, you may need to add information to it, such as labels, values, or reference directions. You may also want to redraw the circuit in a simpler, but equivalent, form. Later in this text you will learn the methods for developing such simplified equivalent circuits.
3. *Think of several solution methods and decide on a way of choosing among them.* This course will help you build a collection of analytical tools, several of which may work on a given problem. But one method may produce fewer equations to be solved than another, or it may require only algebra instead of calculus to reach a solution. Such efficiencies, if you can anticipate them, can streamline your calculations considerably. Having an alternative method in mind also gives you a path to pursue if your first solution attempt bogs down.

4. *Calculate a solution.* Your planning up to this point should have helped you identify a good analytical method and the correct equations for the problem. Now comes the solution of those equations. Paper-and-pencil, calculator, and computer methods are all available for performing the actual calculations of circuit analysis. Efficiency and your instructor's preferences will dictate which tools you should use.
5. *Use your creativity.* If you suspect that your answer is off base or if the calculations seem to go on and on without moving you toward a solution, you should pause and consider alternatives. You may need to revisit your assumptions or select a different solution method. Or you may need to take a less conventional problem-solving approach, such as working backward from a solution. This text provides answers to all of the Assessment Problems and many of the Chapter Problems so that you may work backward when you get stuck. In the real world, you won't be given answers in advance, but you may have a desired problem outcome in mind from which you can work backward. Other creative approaches include allowing yourself to see parallels with other types of problems you've successfully solved, following your intuition or hunches about how to proceed, and simply setting the problem aside temporarily and coming back to it later.
6. *Test your solution.* Ask yourself whether the solution you've obtained makes sense. Does the magnitude of the answer seem reasonable? Is the solution physically realizable? Are the units correct? You may want to rework the problem using an alternative method to validate your original answer and help you develop your intuition about the most efficient solution methods for various kinds of problems. In the real world, safety-critical designs are always checked by several independent means. Getting into the habit of checking your answers will benefit you both as a student and as a practicing engineer.

These problem-solving steps cannot be used as a recipe to solve every problem in this or any other course. You may need to skip, change the order of, or elaborate on certain steps to solve a particular problem. Use these steps as a guideline to develop a problem-solving style that works for you.

## 1.2 The International System of Units

Engineers use quantitative measures to compare theoretical results to experimental results and compare competing engineering designs. Modern engineering is a multidisciplinary profession in which teams of engineers work together on projects, and they can communicate their results in a meaningful way only if they all use the same units of measure. The International System of Units (abbreviated SI) is used by all the major engineering societies and most engineers throughout the world; hence we use it in this text.

The SI units are based on seven *defined* quantities:

- length
- mass
- time
- electric current
- thermodynamic temperature
- amount of substance
- luminous intensity

These quantities, along with the basic unit and symbol for each, are listed in Table 1.1. Although not strictly SI units, the familiar time units